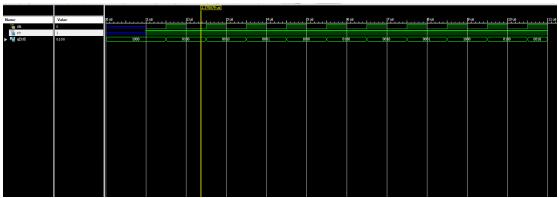
module ringcounter(q,clk,clr);
input clk,clr;
output reg [3:0]q;
initial
begin
q=4'b1000;
end
always@(posedge(clk))
begin
if(clr==0)
begin
q<=4'b0000;
end
else
begin
q[3]<=q[0];
q[2]<=q[3];
q[1]<=q[2];
q[0]<=q[1];
end
end
endmodule



module johnsoncounter(q,clk,clr); input clk,clr; output reg [3:0]q; initial begin q=4'b1000; end always@(posedge(clk)) begin if(clr==0) begin q<=4'b0000; end else begin $q[3]<=^q[0];$ q[2]<=q[3]; q[1]<=q[2]; q[0]<=q[1]; end

end

endmodule

